

Chapitre 1

**E1.6** (a)  $p_a(t) = v_a(t)i_a(t) = 20t^2$

$$w_a = \int_0^{10} p_a(t) dt = \int_0^{10} 20t^2 dt = \left. \frac{20t^3}{3} \right|_0^{10} = \frac{20t^3}{3} = 6667 \text{ J}$$

(b) Notice that the references are opposite to the passive sign convention. Thus we have:

$$p_b(t) = -v_b(t)i_b(t) = 20t - 200$$

$$w_b = \int_0^{10} p_b(t) dt = \int_0^{10} (20t - 200) dt = 10t^2 - 200t \Big|_0^{10} = -1000 \text{ J}$$

**E1.12**  $P = V^2/R \Rightarrow R = V^2/P = 144 \Omega \Rightarrow I = V/R = 120/144 = 0.833 \text{ A}$

**E1.13**  $P = V^2/R \Rightarrow V = \sqrt{PR} = \sqrt{0.25 \times 1000} = 15.8 \text{ V}$   
 $I = V/R = 15.8/1000 = 15.8 \text{ mA}$

**P1.21\*** (a)  $P = -v_a i_a = 30 \text{ W}$  Energy is being absorbed by the element.

(b)  $P = v_b i_b = 30 \text{ W}$  Energy is being absorbed by the element.

(c)  $P = -v_{DE} i_{ED} = -60 \text{ W}$  Energy is being supplied by the element.

**P1.29** The power that can be delivered by the cell is  $p = vi = 0.12 \text{ W}$ . In 75 hours, the energy delivered is  $W = pT = 9 \text{ Whr} = 0.009 \text{ kWhr}$ . Thus the unit cost of the energy is  $Cost = (0.50)/(0.009) = 55.56 \text{ \$/kWhr}$  which is 463 times the typical cost of energy from electric utilities.

**T1.4** (a) Applying KVL, we have  $-V_s + v_1 + v_2 = 0$ . Substituting values given in the problem and solving we find  $v_1 = 8 \text{ V}$ .

(b) Then applying Ohm's law, we have  $i = v_1/R_1 = 8/4 = 2 \text{ A}$ .

(c) Again applying Ohm's law, we have  $R_2 = v_2/i = 4/2 = 2 \Omega$ .

## Chapitre 2

- E2.1** (a)  $R_2$ ,  $R_3$ , and  $R_4$  are in parallel. Furthermore  $R_1$  is in series with the combination of the other resistors. Thus we have:

$$R_{eq} = R_1 + \frac{1}{1/R_2 + 1/R_3 + 1/R_4} = 3 \Omega$$

- (b)  $R_3$  and  $R_4$  are in parallel. Furthermore,  $R_2$  is in series with the combination of  $R_3$ , and  $R_4$ . Finally  $R_1$  is in parallel with the combination of the other resistors. Thus we have:

$$R_{eq} = \frac{1}{1/R_1 + 1/[R_2 + 1/(1/R_3 + 1/R_4)]} = 5 \Omega$$


- (c)  $R_1$  and  $R_2$  are in parallel. Furthermore,  $R_3$ , and  $R_4$  are in parallel. Finally, the two parallel combinations are in series.

$$R_{eq} = \frac{1}{1/R_1 + 1/R_2} + \frac{1}{1/R_3 + 1/R_4} = 52.1 \Omega$$

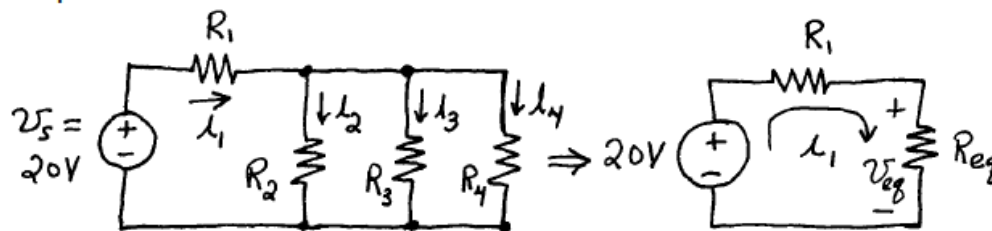- (d)  $R_1$  and  $R_2$  are in series. Furthermore,  $R_3$  is in parallel with the series combination of  $R_1$  and  $R_2$ .

$$R_{eq} = \frac{1}{1/R_3 + 1/(R_1 + R_2)} = 1.5 \text{ k}\Omega$$

- E2.2** (a) First we combine  $R_2$ ,  $R_3$ , and  $R_4$  in parallel. Then  $R_1$  is in series with the parallel combination.




$$R_{eq} = \frac{1}{1/R_2 + 1/R_3 + 1/R_4} = 9.231 \Omega \quad i_1 = \frac{20 \text{ V}}{R_1 + R_{eq}} = \frac{20}{10 + 9.231} = 1.04 \text{ A}$$

$$v_{eq} = R_{eq} i_1 = 9.600 \text{ V} \quad i_2 = v_{eq} / R_2 = 0.480 \text{ A} \quad i_3 = v_{eq} / R_3 = 0.320 \text{ A}$$

$$i_4 = v_{eq} / R_4 = 0.240 \text{ A}$$

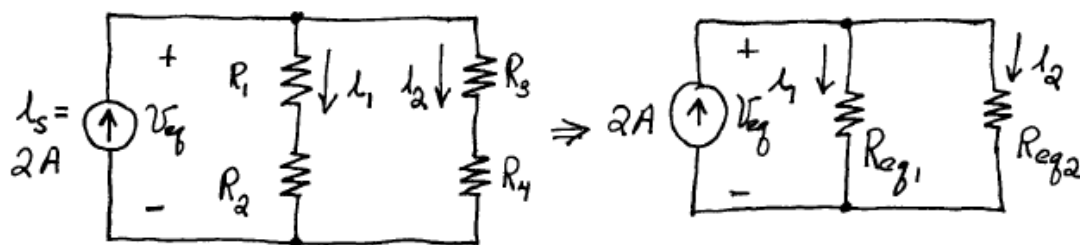
(b)  $R_1$  and  $R_2$  are in series. Furthermore,  $R_3$  and  $R_4$  are in series. Finally, the two series combinations are in parallel.



$$R_{eq1} = R_1 + R_2 = 20 \Omega \quad R_{eq2} = R_3 + R_4 = 20 \Omega \quad R_{eq} = \frac{1}{1/R_{eq1} + 1/R_{eq2}} = 10 \Omega$$

$$v_{eq} = 2 \times R_{eq} = 20 V \quad i_1 = v_{eq} / R_{eq1} = 1 A \quad i_2 = v_{eq} / R_{eq2} = 1 A$$

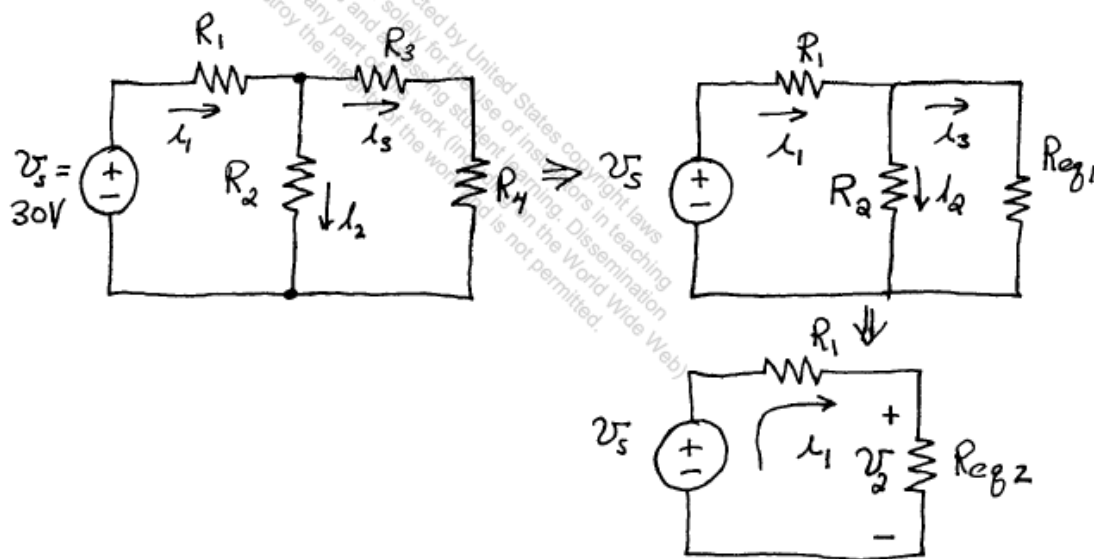(c)  $R_3$  and  $R_4$  are in series. The combination of  $R_3$  and  $R_4$  is in parallel with  $R_2$ . Finally the combination of  $R_2$ ,  $R_3$ , and  $R_4$  is in series with  $R_1$ .



$$R_{eq1} = R_3 + R_4 = 40 \Omega \quad R_{eq2} = \frac{1}{1/R_{eq1} + 1/R_2} = 20 \Omega \quad i_1 = \frac{V_s}{R_1 + R_{eq2}} = 1 A$$

$$v_2 = i_1 R_{eq2} = 20 V \quad i_2 = v_2 / R_2 = 0.5 A \quad i_3 = v_2 / R_{eq1} = 0.5 A$$

**E2.3** (a)  $v_1 = v_s \frac{R_1}{R_1 + R_2 + R_3 + R_4} = 10 V$ .  $v_2 = v_s \frac{R_2}{R_1 + R_2 + R_3 + R_4} = 20 V$ .

Similarly, we find  $v_3 = 30 V$  and  $v_4 = 60 V$ .

(b) First combine  $R_2$  and  $R_3$  in parallel:  $R_{eq} = 1/(1/R_2 + 1/R_3) = 2.917 \Omega$

Then we have  $v_1 = v_s \frac{R_1}{R_1 + R_{eq} + R_4} = 6.05 \text{ V}$ . Similarly, we find

$$v_2 = v_s \frac{R_{eq}}{R_1 + R_{eq} + R_4} = 5.88 \text{ V and } v_4 = 8.07 \text{ V}.$$

**E2.4** (a) First combine  $R_1$  and  $R_2$  in series:  $R_{eq} = R_1 + R_2 = 30 \Omega$ . Then we have

$$i_1 = i_s \frac{R_3}{R_3 + R_{eq}} = \frac{15}{15 + 30} = 1 \text{ A and } i_3 = i_s \frac{R_{eq}}{R_3 + R_{eq}} = \frac{30}{15 + 30} = 2 \text{ A}.$$

(b) The current division principle applies to two resistances in parallel. Therefore, to determine  $i_1$ , first combine  $R_2$  and  $R_3$  in parallel:  $R_{eq} =$

$$1/(1/R_2 + 1/R_3) = 5 \Omega. \text{ Then we have } i_1 = i_s \frac{R_{eq}}{R_1 + R_{eq}} = \frac{5}{10 + 5} = 1 \text{ A}.$$

Similarly,  $i_2 = 1 \text{ A}$  and  $i_3 = 1 \text{ A}$ .

**P2.1\*** (a)  $R_{eq} = 20 \Omega$  (b)  $R_{eq} = 23 \Omega$

**P2.2\*** We have  $4 + \frac{1}{1/20 + 1/R_x} = 8$  which yields  $R_x = 5 \Omega$ .

## Chapitre 5

- E5.1** (a) We are given  $v(t) = 150 \cos(200\pi t - 30^\circ)$ . The angular frequency is the coefficient of  $t$  so we have  $\omega = 200\pi$  radian/s. Then

$$f = \omega / 2\pi = 100 \text{ Hz} \quad T = 1/f = 10 \text{ ms}$$

$$V_{rms} = V_m / \sqrt{2} = 150 / \sqrt{2} = 106.1 \text{ V}$$

Furthermore,  $v(t)$  attains a positive peak when the argument of the cosine function is zero. Thus keeping in mind that  $\omega t$  has units of radians, the positive peak occurs when

$$\omega t_{\max} = 30 \times \frac{\pi}{180} \Rightarrow t_{\max} = 0.8333 \text{ ms}$$

(b)  $P_{avg} = V_{rms}^2 / R = 225 \text{ W}$

(c) A plot of  $v(t)$  is shown in Figure 5.4 in the book.

**E5.3**  $\omega = 2\pi f \cong 377 \text{ radian/s} \quad T = 1/f \cong 16.67 \text{ ms} \quad V_m = V_{rms} \sqrt{2} \cong 155.6 \text{ V}$

The period corresponds to  $360^\circ$  therefore 5 ms corresponds to a phase angle of  $(5/16.67) \times 360^\circ = 108^\circ$ . Thus the voltage is

$$v(t) = 155.6 \cos(377t - 108^\circ)$$

**P5.5\*** Sinusoidal voltages can be expressed in the form  $v(t) = V_m \cos(\omega t + \theta)$ . The peak voltage is  $V_m = \sqrt{2} V_{rms} = \sqrt{2} \times 20 = 28.28 \text{ V}$ . The frequency is  $f = 1/T = 10 \text{ kHz}$  and the angular frequency is  $\omega = 2\pi f = 2\pi \times 10^4$  radians/s. The phase corresponding to a time interval of  $\Delta t = 20 \mu\text{s}$  is  $\theta = (\Delta t / T) \times 360^\circ = 72^\circ$ . Thus we have  $v(t) = 28.28 \cos(2\pi \times 10^4 t - 72^\circ) \text{ V}$ .

**P5.11\*** 
$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt} = \sqrt{\frac{1}{2} \int_0^1 25 dt} = 3.536 \text{ V}$$

**P5.13\*** 
$$I_{rms} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt} = \sqrt{\frac{1}{4} \left( \int_0^2 4 dt + \int_2^4 1 dt \right)} = 1.581 \text{ A}$$


**T5.1** 
$$I_{rms} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt} = \sqrt{\frac{1}{3} \int_0^2 (3t)^2 dt} = \sqrt{t^3 \Big|_0^2} = \sqrt{8} = 2.828 \text{ A}$$
  

$$P = I_{rms}^2 R = 8(50) = 400 \text{ W}$$
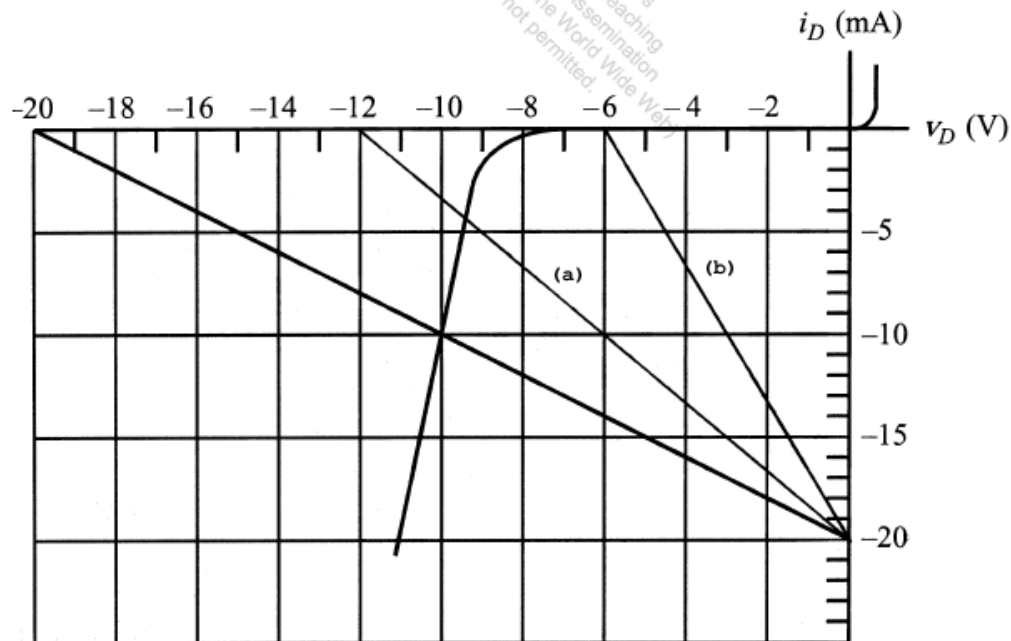
## Chapitre 9

Attention cette solution est une solution avancée. La droite de charge ne fait pas partie de la matière de l'APP1.

- E9.4** Following the methods of Example 10.4 in the book, we determine that:  
(a) For  $R_L = 1200\ \Omega$ ,  $R_T = 600\ \Omega$ , and  $V_T = 12\text{ V}$ .  
(b) For  $R_L = 400\ \Omega$ ,  $R_T = 300\ \Omega$ , and  $V_T = 6\text{ V}$ .  
The corresponding load lines are:




At the intersections of the load lines with the diode characteristic we find (a)  $v_L = -v_D \cong 9.4\text{ V}$ ; (b)  $v_L = -v_D \cong 6.0\text{ V}$ .

Attention, ce problème est aussi un problème avancé. Vous devriez être en mesure de résoudre, de façon plus simple, ce problème.

**E9.5** Writing a KVL equation for the loop consisting of the source, the resistor, and the load, we obtain:

$$15 = 100(i_L - i_D) - v_D$$

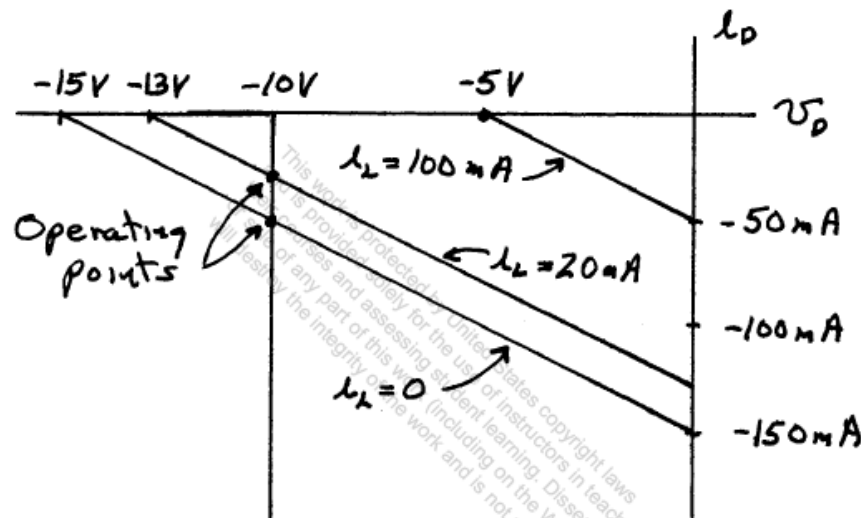
The corresponding load lines for the three specified values of  $i_L$  are shown:




At the intersections of the load lines with the diode characteristic, we find (a)  $v_o = -v_D = 10$  V; (b)  $v_o = -v_D = 10$  V; (c)  $v_o = -v_D = 5$  V. Notice that the regulator is effective only for values of load current up to 50 mA.






P9.1

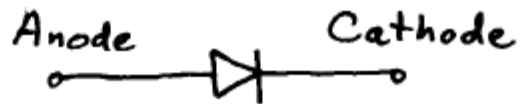

P9.2

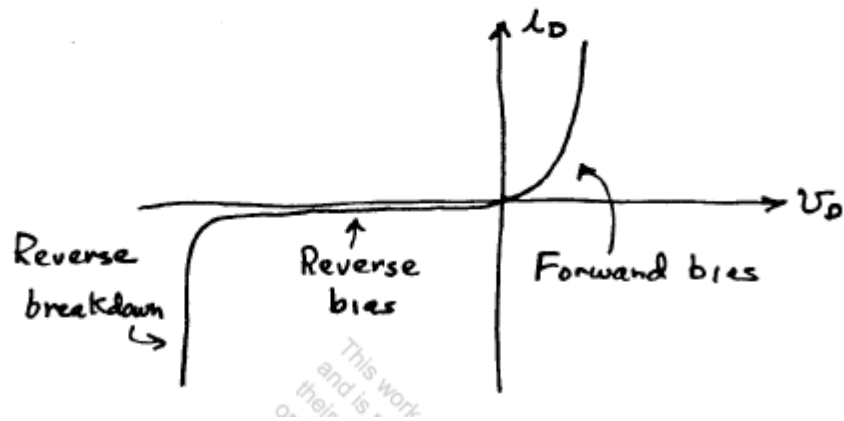

P9.6\*

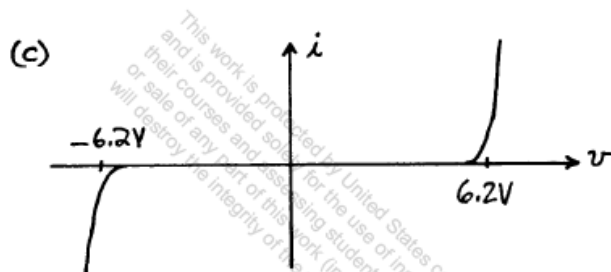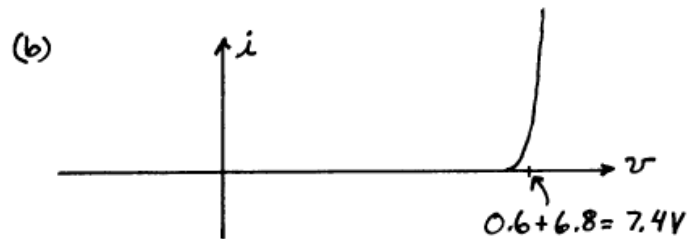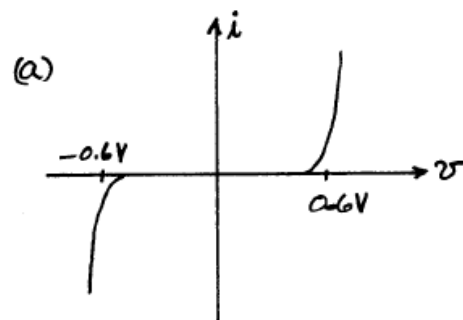



**P9.25** A Zener diode is a diode intended for operation in the reverse breakdown region. It is typically used to provide a source of constant voltage. The volt-ampere characteristic of an ideal 5.8-V Zener diode is:

