

Chapitre 1

E1.6 (a) $p_a(t) = v_a(t)i_a(t) = 20t^2$

$$w_a = \int_0^{10} p_a(t) dt = \int_0^{10} 20t^2 dt = \frac{20t^3}{3} \bigg|_0^{10} = \frac{20t^3}{3} = 6667 \text{ J}$$

(b) Notice that the references are opposite to the passive sign convention. Thus we have:

$$p_b(t) = -v_b(t)i_b(t) = 20t - 200$$

$$w_b = \int_0^{10} p_b(t) dt = \int_0^{10} (20t - 200) dt = 10t^2 - 200t \bigg|_0^{10} = -1000 \text{ J}$$

E1.12 $P = V^2/R \Rightarrow R = V^2/P = 144 \Omega \Rightarrow I = V/R = 120/144 = 0.833 \text{ A}$

E1.13 $P = V^2/R \Rightarrow V = \sqrt{PR} = \sqrt{0.25 \times 1000} = 15.8 \text{ V}$
 $I = V/R = 15.8/1000 = 15.8 \text{ mA}$

P1.21* (a) $P = -v_a i_a = 30 \text{ W}$ Energy is being absorbed by the element.

(b) $P = v_b i_b = 30 \text{ W}$ Energy is being absorbed by the element.

(c) $P = -v_d i_d = -60 \text{ W}$ Energy is being supplied by the element.

P1.30 The power that can be delivered by the cell is $p = vi = 0.45 \text{ W}$. In 10 hours, the energy delivered is $W = pT = 4.5 \text{ Whr} = 0.0045 \text{ kWhr}$. Thus, the unit cost of the energy is $Cost = (1.95)/(0.0045) = 433.33 \text{ \$/kWhr}$ which is 3611 times the typical cost of energy from electric utilities.

T1.4 (a) Applying KVL, we have $-V_s + v_1 + v_2 = 0$. Substituting values given in the problem and solving we find $v_1 = 8 \text{ V}$.

(b) Then applying Ohm's law, we have $i = v_1/R_1 = 8/4 = 2 \text{ A}$.

(c) Again applying Ohm's law, we have $R_2 = v_2/i = 4/2 = 2 \Omega$.

Chapitre 2

- E2.1** (a) R_2 , R_3 , and R_4 are in parallel. Furthermore R_1 is in series with the combination of the other resistors. Thus we have:

$$R_{eq} = R_1 + \frac{1}{1/R_2 + 1/R_3 + 1/R_4} = 3 \Omega$$

- (b) R_3 and R_4 are in parallel. Furthermore, R_2 is in series with the combination of R_3 , and R_4 . Finally R_1 is in parallel with the combination of the other resistors. Thus we have:

$$R_{eq} = \frac{1}{1/R_1 + 1/[R_2 + 1/(1/R_3 + 1/R_4)]} = 5 \Omega$$


- (c) R_1 and R_2 are in parallel. Furthermore, R_3 , and R_4 are in parallel. Finally, the two parallel combinations are in series.

$$R_{eq} = \frac{1}{1/R_1 + 1/R_2} + \frac{1}{1/R_3 + 1/R_4} = 52.1 \Omega$$

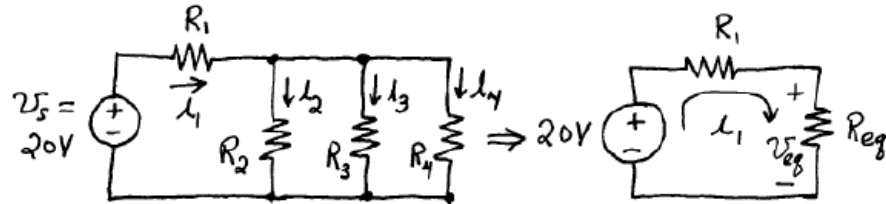- (d) R_1 and R_2 are in series. Furthermore, R_3 is in parallel with the series combination of R_1 and R_2 .

$$R_{eq} = \frac{1}{1/R_3 + 1/(R_1 + R_2)} = 1.5 \text{ k}\Omega$$

- E2.2** (a) First we combine R_2 , R_3 , and R_4 in parallel. Then R_1 is in series with the parallel combination.




$$R_{eq} = \frac{1}{1/R_2 + 1/R_3 + 1/R_4} = 9.231 \Omega \quad i_1 = \frac{20 \text{ V}}{R_1 + R_{eq}} = \frac{20}{10 + 9.231} = 1.04 \text{ A}$$

$$v_{eq} = R_{eq} i_1 = 9.600 \text{ V} \quad i_2 = v_{eq} / R_2 = 0.480 \text{ A} \quad i_3 = v_{eq} / R_3 = 0.320 \text{ A}$$

$$i_4 = v_{eq} / R_4 = 0.240 \text{ A}$$

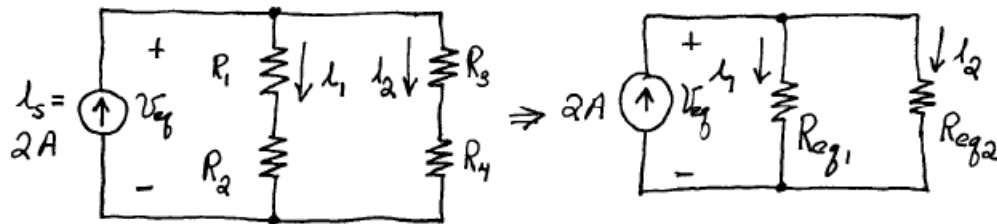
(b) R_1 and R_2 are in series. Furthermore, R_3 and R_4 are in series. Finally, the two series combinations are in parallel.



$$R_{eq1} = R_1 + R_2 = 20 \Omega \quad R_{eq2} = R_3 + R_4 = 20 \Omega \quad R_{eq} = \frac{1}{1/R_{eq1} + 1/R_{eq2}} = 10 \Omega$$

$$V_{eq} = 2 \times R_{eq} = 20 \text{ V} \quad i_1 = V_{eq} / R_{eq1} = 1 \text{ A} \quad i_2 = V_{eq} / R_{eq2} = 1 \text{ A}$$

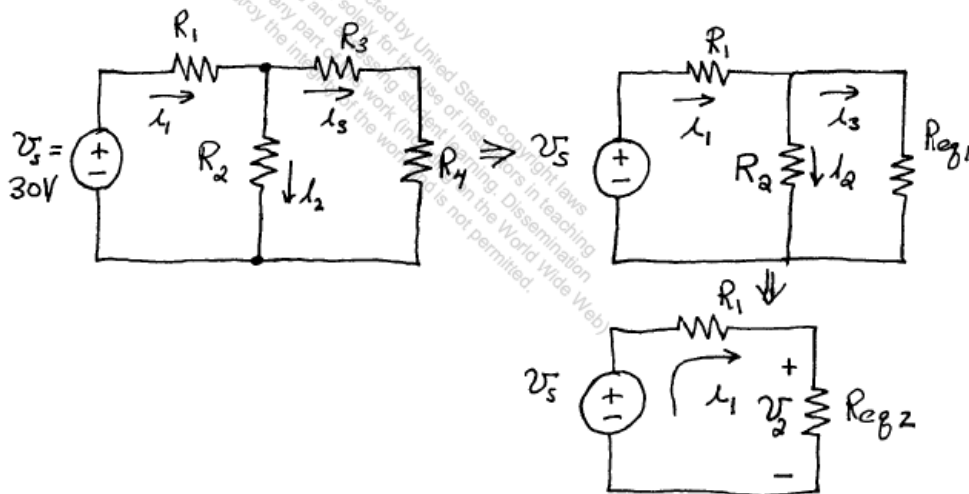(c) R_3 and R_4 are in series. The combination of R_3 and R_4 is in parallel with R_2 . Finally the combination of R_2 , R_3 , and R_4 is in series with R_1 .



$$R_{eq1} = R_3 + R_4 = 40 \Omega \quad R_{eq2} = \frac{1}{1/R_{eq1} + 1/R_2} = 20 \Omega \quad i_1 = \frac{V_s}{R_1 + R_{eq2}} = 1 \text{ A}$$

$$V_2 = i_1 R_{eq2} = 20 \text{ V} \quad i_2 = V_2 / R_2 = 0.5 \text{ A} \quad i_3 = V_2 / R_{eq1} = 0.5 \text{ A}$$

E2.3 (a) $V_1 = V_s \frac{R_1}{R_1 + R_2 + R_3 + R_4} = 10 \text{ V}$. $V_2 = V_s \frac{R_2}{R_1 + R_2 + R_3 + R_4} = 20 \text{ V}$.

Similarly, we find $V_3 = 30 \text{ V}$ and $V_4 = 60 \text{ V}$.

(b) First combine R_2 and R_3 in parallel: $R_{eq} = 1/(1/R_2 + 1/R_3) = 2.917 \Omega$.

Then we have $v_1 = v_s \frac{R_1}{R_1 + R_{eq} + R_4} = 6.05 \text{ V}$. Similarly, we find

$$v_2 = v_s \frac{R_{eq}}{R_1 + R_{eq} + R_4} = 5.88 \text{ V and } v_4 = 8.07 \text{ V}.$$

E2.4 (a) First combine R_1 and R_2 in series: $R_{eq} = R_1 + R_2 = 30 \Omega$. Then we have

$$i_1 = i_s \frac{R_3}{R_3 + R_{eq}} = \frac{15}{15 + 30} = 1 \text{ A and } i_3 = i_s \frac{R_{eq}}{R_3 + R_{eq}} = \frac{30}{15 + 30} = 2 \text{ A}.$$

(b) The current division principle applies to two resistances in parallel. Therefore, to determine i_1 , first combine R_2 and R_3 in parallel: $R_{eq} =$

$$1/(1/R_2 + 1/R_3) = 5 \Omega. \text{ Then we have } i_1 = i_s \frac{R_{eq}}{R_1 + R_{eq}} = \frac{5}{10 + 5} = 1 \text{ A}.$$

Similarly, $i_2 = 1 \text{ A}$ and $i_3 = 1 \text{ A}$.

P2.1* (a) $R_{eq} = 20 \Omega$ (b) $R_{eq} = 23 \Omega$

P2.2* We have $4 + \frac{1}{1/20 + 1/R_x} = 8$ which yields $R_x = 5 \Omega$.

Chapitre 5

- E5.1** (a) We are given $v(t) = 150 \cos(200\pi t - 30^\circ)$. The angular frequency is the coefficient of t so we have $\omega = 200\pi$ radian/s. Then

$$f = \omega / 2\pi = 100 \text{ Hz} \quad T = 1/f = 10 \text{ ms}$$

$$V_{rms} = V_m / \sqrt{2} = 150 / \sqrt{2} = 106.1 \text{ V}$$

Furthermore, $v(t)$ attains a positive peak when the argument of the cosine function is zero. Thus keeping in mind that ωt has units of radians, the positive peak occurs when

$$\omega t_{\max} = 30 \times \frac{\pi}{180} \Rightarrow t_{\max} = 0.8333 \text{ ms}$$

(b) $P_{avg} = V_{rms}^2 / R = 225 \text{ W}$

(c) A plot of $v(t)$ is shown in Figure 5.4 in the book.

E5.3 $\omega = 2\pi f = 377 \text{ radian/s} \quad T = 1/f = 16.67 \text{ ms} \quad V_m = V_{rms} \sqrt{2} = 155.6 \text{ V}$

The period corresponds to 360° therefore 5 ms corresponds to a phase angle of $(5/16.67) \times 360^\circ = 108^\circ$. Thus the voltage is

$$v(t) = 155.6 \cos(377t - 108^\circ)$$

- P5.6*** Sinusoidal voltages can be expressed in the form $v(t) = V_m \cos(\omega t + \theta)$. The peak voltage is $V_m = \sqrt{2} V_{rms} = \sqrt{2} \times 20 = 28.28 \text{ V}$. The frequency is $f = 1/T = 10 \text{ kHz}$ and the angular frequency is $\omega = 2\pi f = 2\pi 10^4$ radians/s. The phase corresponding to a time interval of $\Delta t = 20 \mu\text{s}$ is $\theta = (\Delta t / T) \times 360^\circ = 72^\circ$. Thus, we have $v(t) = 28.28 \cos(2\pi 10^4 t - 72^\circ) \text{ V}$.

P5.12*
$$I_{rms} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt} = \sqrt{\frac{1}{4} \left(\int_0^2 25 dt + \int_2^4 4 dt \right)} = 3.808 \text{ A}$$

P5.13*
$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt} = \sqrt{\frac{1}{2} \int_0^1 15^2 dt} = 10.61 \text{ V}$$


T5.1
$$I_{rms} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt} = \sqrt{\frac{1}{3} \int_0^2 (3t)^2 dt} = \sqrt{t^3 \Big|_0^2} = \sqrt{8} = 2.828 \text{ A}$$

$$P = I_{rms}^2 R = 8(50) = 400 \text{ W}$$

Chapitre 10

Attention cette solution est une solution avancée. La droite de charge ne fait pas partie de la matière de l'APP1.

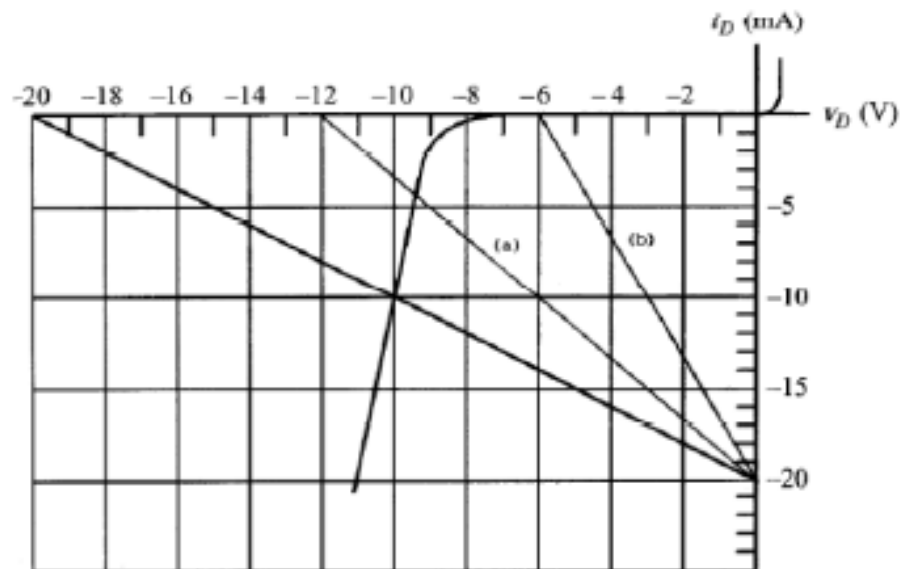- E10.4** Following the methods of Example 10.4 in the book, we determine that:
- (a) For $R_L = 1200\ \Omega$, $R_T = 600\ \Omega$, and $V_T = 12\text{ V}$.
 - (b) For $R_L = 400\ \Omega$, $R_T = 300\ \Omega$, and $V_T = 6\text{ V}$.
- The corresponding load lines are:




At the intersections of the load lines with the diode characteristic we find (a) $v_L = -v_D \approx 9.4\text{ V}$; (b) $v_L = -v_D \approx 6.0\text{ V}$.

Attention, ce problème est aussi un problème avancé. Vous devriez être en mesure résoudre de façon plus simple ce problème.

E10.5 Writing a KVL equation for the loop consisting of the source, the resistor, and the load, we obtain:


$$15 = 100(i_L - i_D) - v_D$$

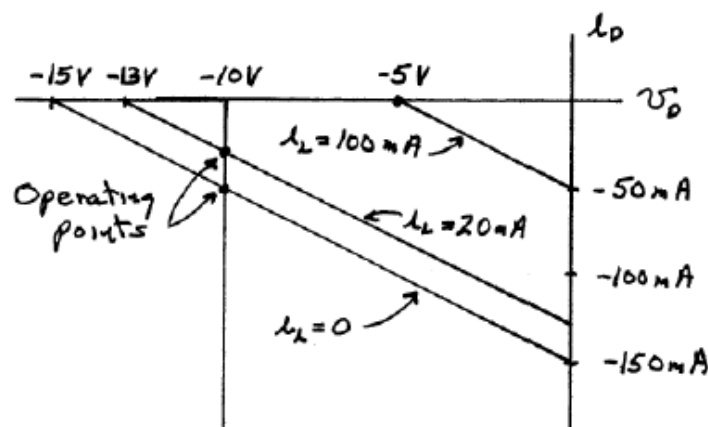The corresponding load lines for the three specified values of i_L are shown:




At the intersections of the load lines with the diode characteristic, we find (a) $v_o = -v_D = 10 \text{ V}$; (b) $v_o = -v_D = 10 \text{ V}$; (c) $v_o = -v_D = 5 \text{ V}$. Notice that the regulator is effective only for values of load current up to 50 mA.


P10.2

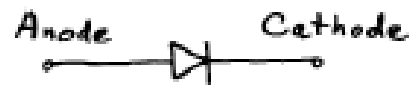

P10.3

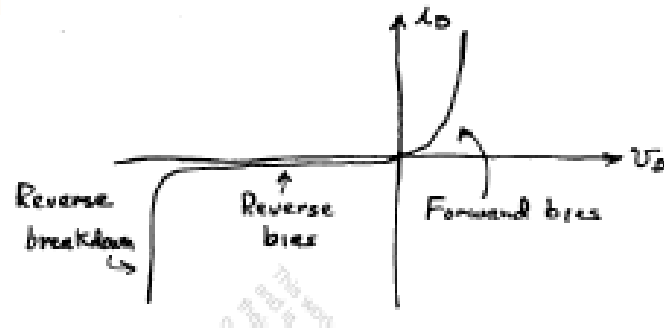

P10.8

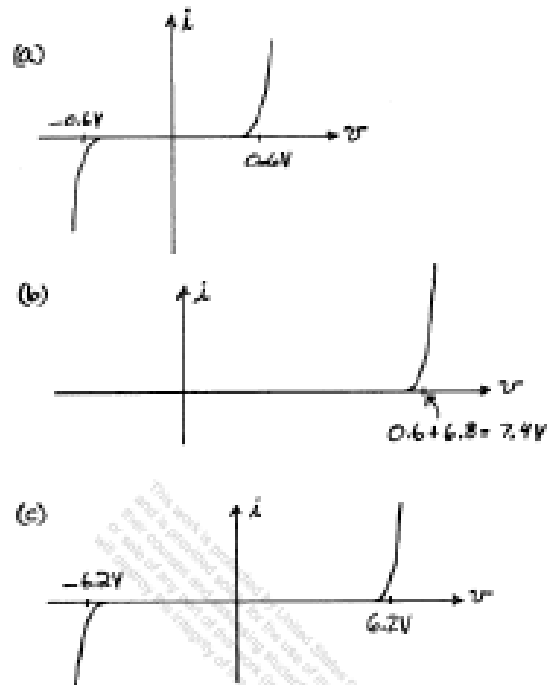

P10.22

A Zener diode is a diode intended for operation in the reverse breakdown region. It is typically used to provide a source of constant voltage. The volt-ampere characteristic of an ideal 5.8-V Zener diode is:

